



## **CHAPTER 4 Bipolar Junction Transistors**

**Xuewei Pan, PhD, Associate Professor**

# **CHAPTER 4 Bipolar Junction Transistors**

## **4.1 Bipolar Junction Transistors Structure**


## **4.2 Basic BJT Operation**

## **4.3 BJT Characteristics and Parameters**

# 4.1 Bipolar Junction Transistors (BJT) Structure

- The **BJT** is constructed with three doped semiconductor regions separated by two pn junctions, as shown in the epitaxial planar structure in Figure 4–1(a). The three regions are called **emitter**, **base**, and **collector**.
- Physical representations of the two types of BJTs are shown in Figure 4–1(b) and (c). One type consists of two n regions separated by a p region (**npn**), and the other type consists of two p regions separated by an n region (**pnp**).

The term bipolar refers to the use of both holes and electrons as current carriers in the transistor structure.

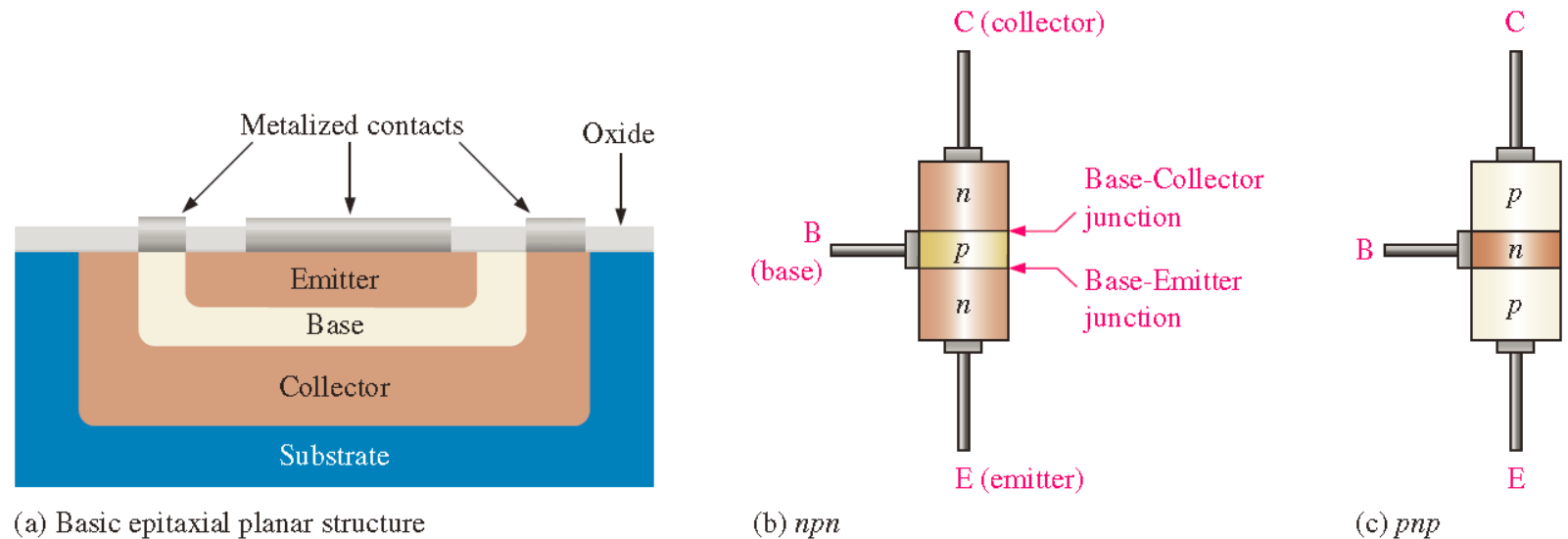


**FIGURE 4-1**

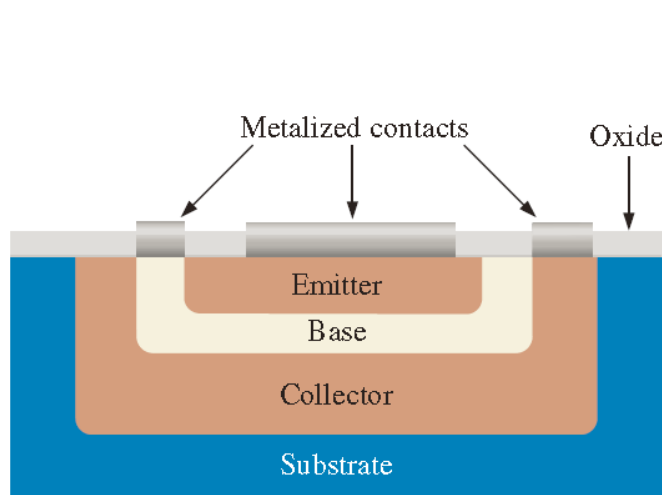
BJT construction. The substrate is a physical supporting material for the transistor.

# Bipolar Junction Transistors (BJT) Structure


- The **pn** junction joining the base region and the emitter region is called the **base-emitter junction**. The pn junction joining the base region and the collector region is called the **base-collector junction**, as indicated in Figure 4–1(b). A lead connects to each of the three regions, as shown. These leads are labeled **E, B, and C** for **emitter, base, and collector**, respectively.
- The **base region is lightly doped** and very thin compared to the **heavily doped emitter** and the **moderately doped collector** regions.




(a) Basic epitaxial planar structure

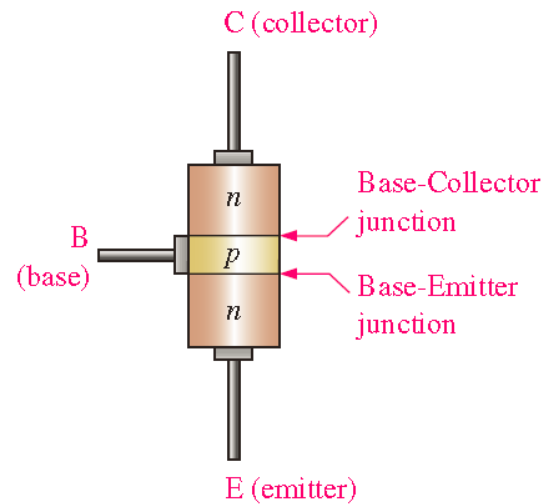


(b) npn

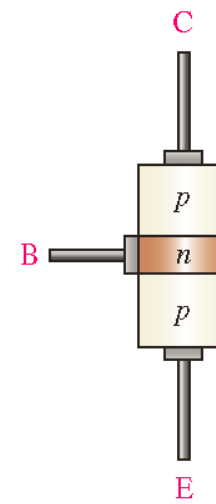

(c) pnp

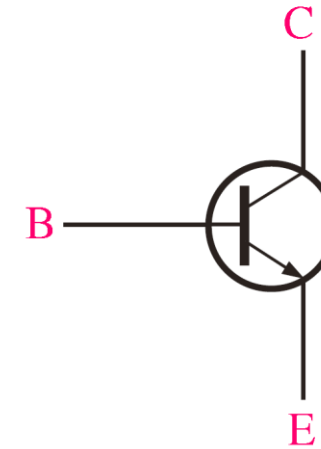

(a) npn

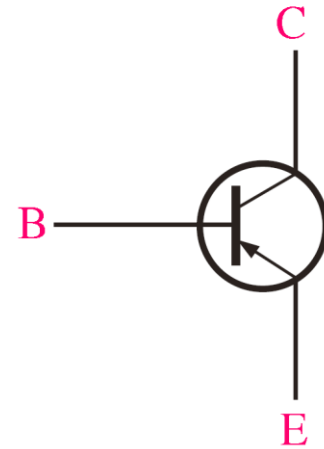

(b) pnp


**FIGURE 4-1**

BJT construction. The substrate is a physical supporting material for the transistor.

**FIGURE 4-2** Standard BJT (bipolar junction transistor) symbols

## 4.2 Basic BJT Operation

- Biassing:** Figure 4–3 shows a bias arrangement for both npn and pnp BJTs for operation as an amplifier. Notice that in both cases the base-emitter (BE) junction is forward-biased and the base-collector (BC) junction is reverse-biased.

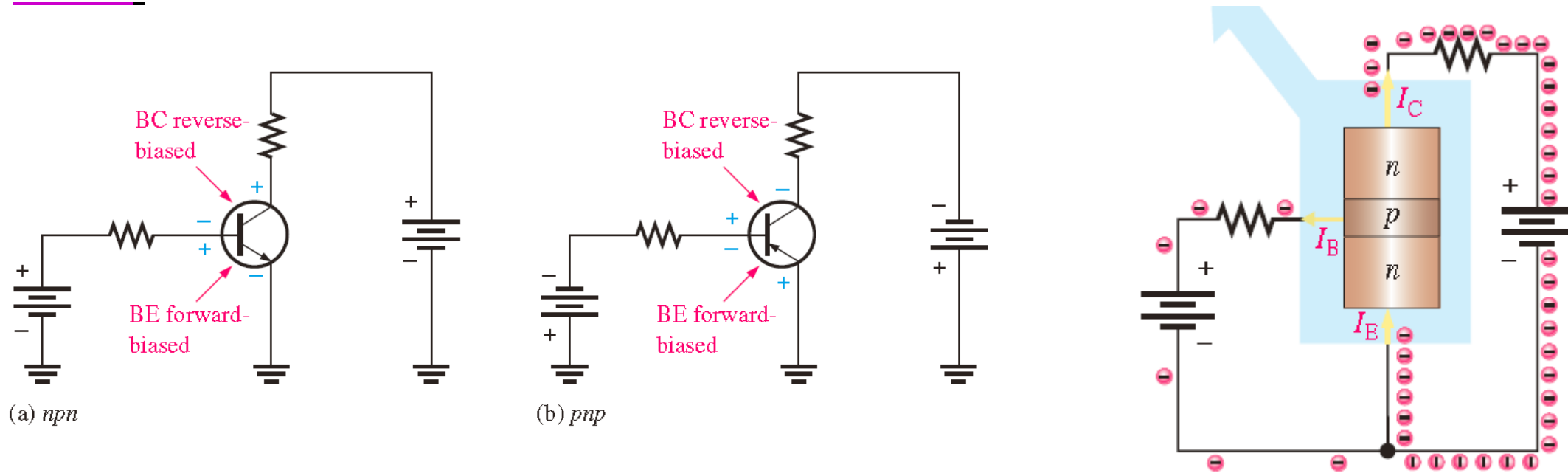


**FIGURE 4-3** Forward-reverse bias of a BJT.

# Basic BJT Operation

- Free electrons easily diffuse through the forward biased BE junction into the lightly doped and very thin p-type base region. A small percentage of the total number of free electrons injected into the base region recombine with holes.

The rest free electrons move toward the reverse-biased BC junction, they are swept across into the collector region by the attraction of the positive collector supply voltage.

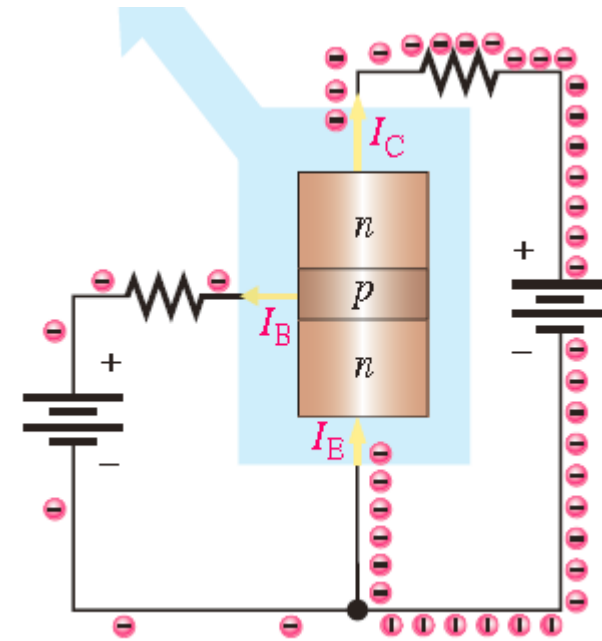


**FIGURE 4-4** BJT operation showing electro flow.

# Transistor Currents

- The **directions of the currents** in an npn transistor and its schematic symbol are as shown in Figure 4–5(a);
- These diagrams show that the emitter current ( $I_E$ ) is the sum of the collector current ( $I_C$ ) and the base current ( $I_B$ ), expressed as follows:

$$I_E = I_C + I_B$$

As mentioned before,  $I_B$  is very small compared to  $I_E$  or  $I_C$ . The capital-letter subscripts indicate dc values.

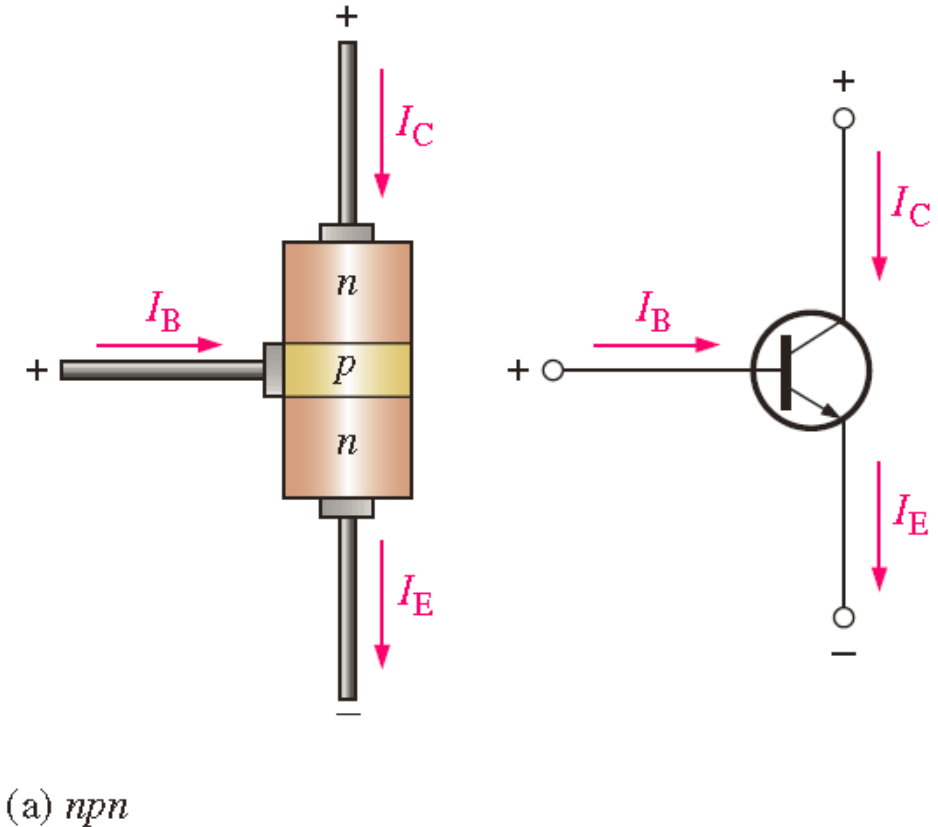

**FIGURE 4-5** Transistor currents


## 4-3 BJT Characteristics and Parameters

$I_B / \text{mA}$	-0.01	0	0.02	0.04	0.06	0.08	0.1
$I_C / \text{mA}$	0.001	0.01	0.7	1.5	2.3	3.1	3.95
$I_E / \text{mA}$	0	0.01	0.72	1.54	2.36	3.18	4.05

$$I_E = I_C + I_B \quad I_C \gg I_B$$

- BJT has **current amplifier** function. Current amplify gain is almost constant within acceptable varying range.
- The dc current **gain** of a transistor is the ratio of the dc collector current ( $I_C$ ) to the dc base current ( $I_B$ ) and is designated dc beta ( $\beta_{DC}$ ).

$$\beta_{DC} = \frac{I_C}{I_B}$$

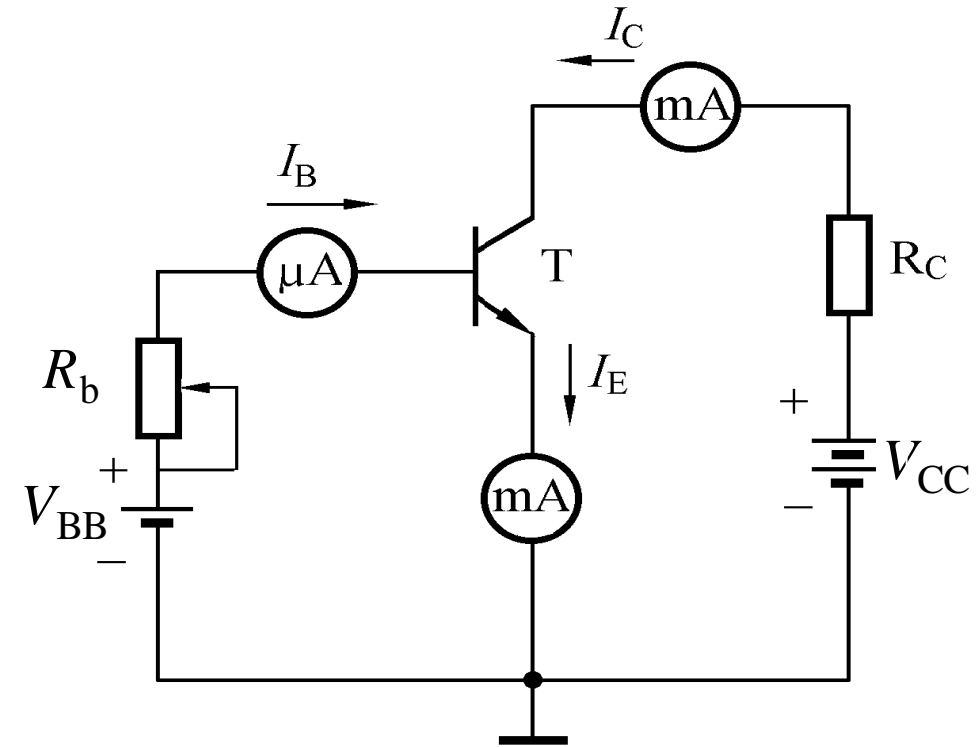

**FIGURE 4-6** Testing circuit of Forward-reverse biased BJT.

Through varying the resistor,  $I_B$ ,  $I_C$  and  $I_E$  can be varied correspondingly.



# Example

## EXAMPLE 4–1

Determine the dc current gain  $\beta_{DC}$  and the emitter current  $I_E$  for a transistor where  $I_B = 50 \mu\text{A}$  and  $I_C = 3.65 \text{ mA}$ .

*Solution*

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{3.65 \text{ mA}}{50 \mu\text{A}} = 73$$


$$I_E = I_C + I_B = 3.65 \text{ mA} + 50 \mu\text{A} = 3.70 \text{ mA}$$

*Related Problem\**

A certain transistor has a  $\beta_{DC}$  of 200. When the base current is  $50 \mu\text{A}$ , determine the collector current.

# Transistor DC Model

- You can view the unsaturated BJT as a device with a **current input and a dependent current source** in the output circuit, as shown in Figure 4–7 for an *npn transistor*.
- The input circuit is a **forward-biased diode** through which there is base current. The output circuit is a **dependent current source** (diamond-shaped element) with a value that is dependent on the base current,  $I_B$ , and equal to  $\beta_{DC}I_B$ .

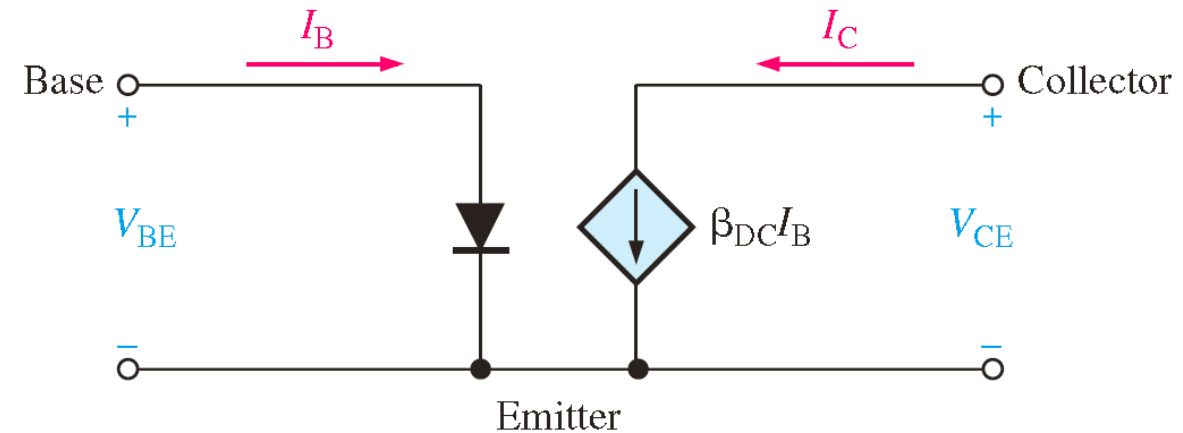

**FIGURE 4-7**

Ideal dc model of an *npn* transistor

# BJT Circuit Analysis

$I_B$ : dc base current

$I_E$ : dc emitter current


$I_C$ : dc collector current

$V_{BE}$ : dc voltage at base with respect to emitter

$V_{CB}$ : dc voltage at collector with respect to base

$V_{CE}$ : dc voltage at collector with respect to emitter

The base-bias voltage source,  $V_{BB}$ , forward-biases the base-emitter junction, and the collector-bias voltage source,  $V_{CC}$ , reverse-biases the base-collector junction. When the base-emitter junction is forward-biased, it is like a forward-biased diode and has a nominal forward voltage drop of  $V_{BE} \cong 0.7 \text{ V}$

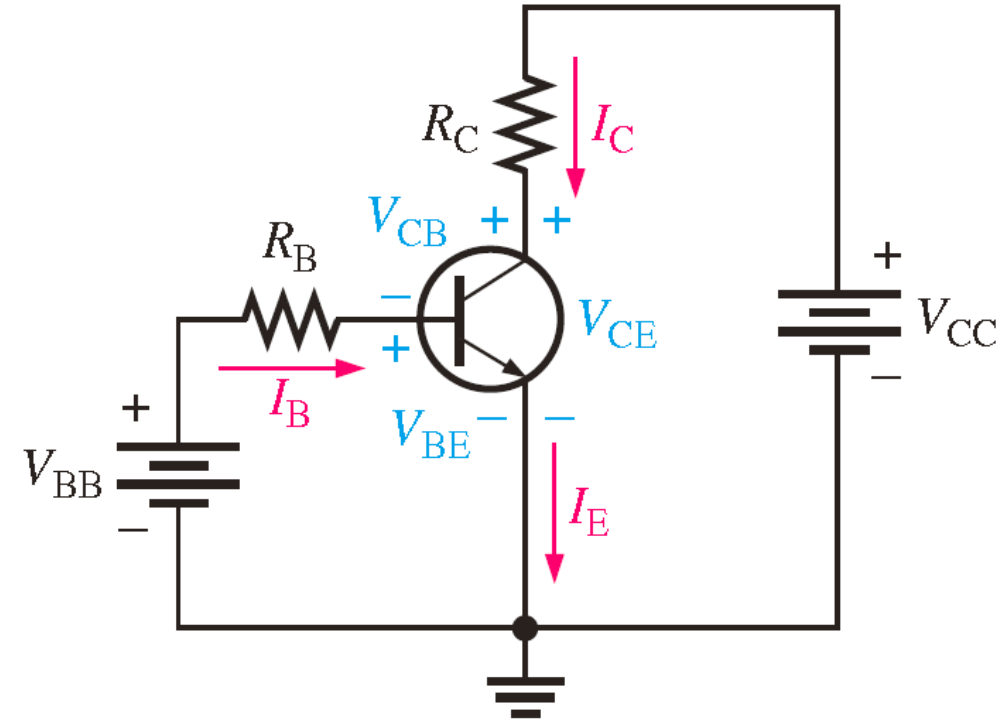

**FIGURE 4-8**

Transistor currents and voltages.

# BJT Circuit Analysis

Since the emitter is at ground (0 V), by Kirchhoff's voltage law, the voltage across  $R_B$  is

$$V_{R_B} = V_{BB} - V_{BE}$$

Also, by Ohm's law,


$$V_{R_B} = I_B R_B$$

Substituting for  $V_{R_B}$  yields

$$I_B R_B = V_{BB} - V_{BE}$$

Solving for  $I_B$ ,

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

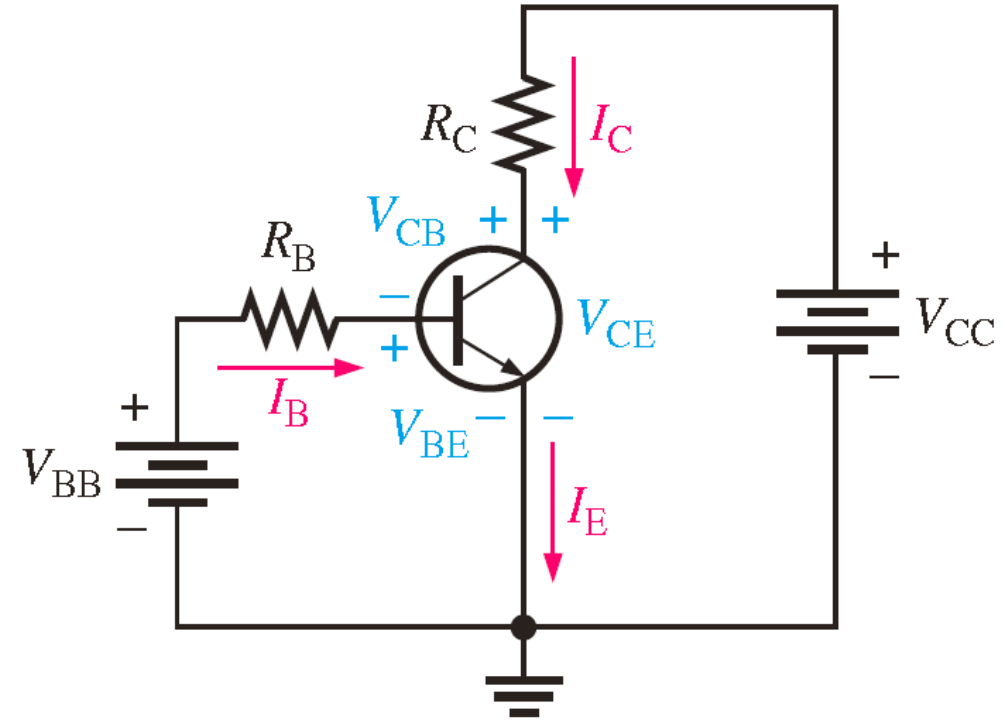

**FIGURE 4-8**

Transistor currents and voltages.

# BJT Circuit Analysis

The voltage at the collector with respect to the grounded emitter is

$$V_{CE} = V_{CC} - V_{R_C}$$

Since the drop across  $R_C$  is

$$V_{R_C} = I_C R_C$$


the voltage at the collector with respect to the emitter can be written

$$V_{CE} = V_{CC} - I_C R_C$$

where  $I_C = \beta_{DC} I_B$ .

The voltage across the reverse-biased collector-base junction is

$$V_{CB} = V_{CE} - V_{BE}$$

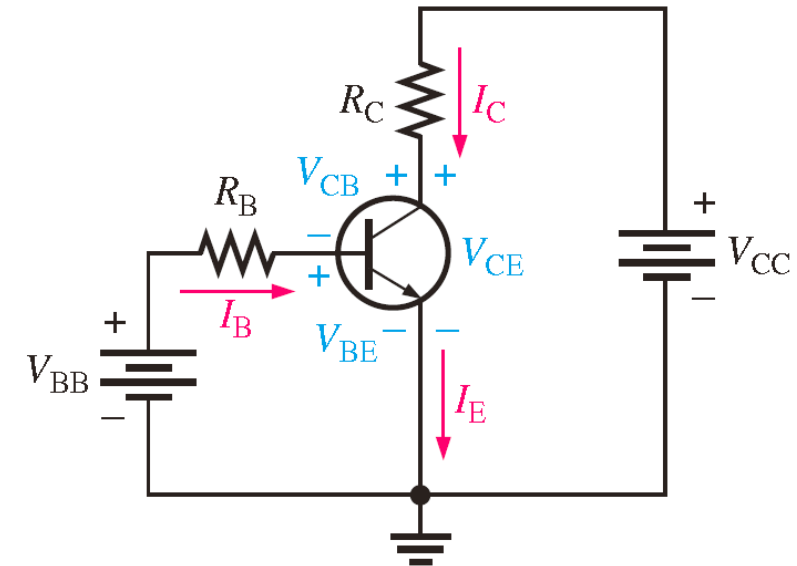

**FIGURE 4-8**


Transistor currents and voltages.

# Example

## EXAMPLE 4–2

Determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{BE}$ ,  $V_{CE}$ , and  $V_{CB}$  in the circuit of Figure 4–9. The transistor has a  $\beta_{DC} = 150$ .

► FIGURE 4–9

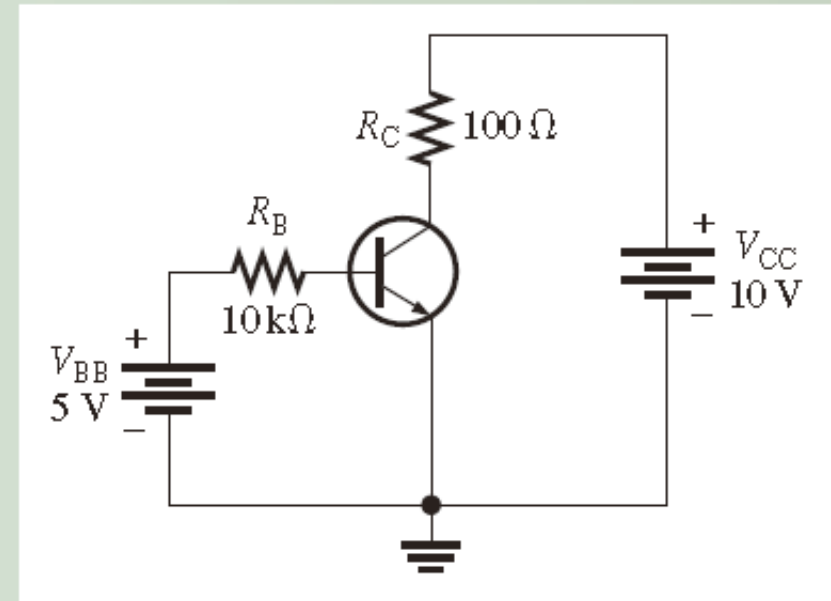

# Example

**Solution** From Equation 4–3,  $V_{BE} \cong 0.7 \text{ V}$ . Calculate the base, collector, and emitter currents as follows:

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 430 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (150)(430 \mu\text{A}) = 64.5 \text{ mA}$$

$$I_E = I_C + I_B = 64.5 \text{ mA} + 430 \mu\text{A} = 64.9 \text{ mA}$$

Solve for  $V_{CE}$  and  $V_{CB}$ .


$$V_{CE} = V_{CC} - I_C R_C = 10 \text{ V} - (64.5 \text{ mA})(100 \Omega) = 10 \text{ V} - 6.45 \text{ V} = 3.55 \text{ V}$$

$$V_{CB} = V_{CE} - V_{BE} = 3.55 \text{ V} - 0.7 \text{ V} = 2.85 \text{ V}$$


Since the collector is at a higher voltage than the base, the collector-base junction is reverse-biased.
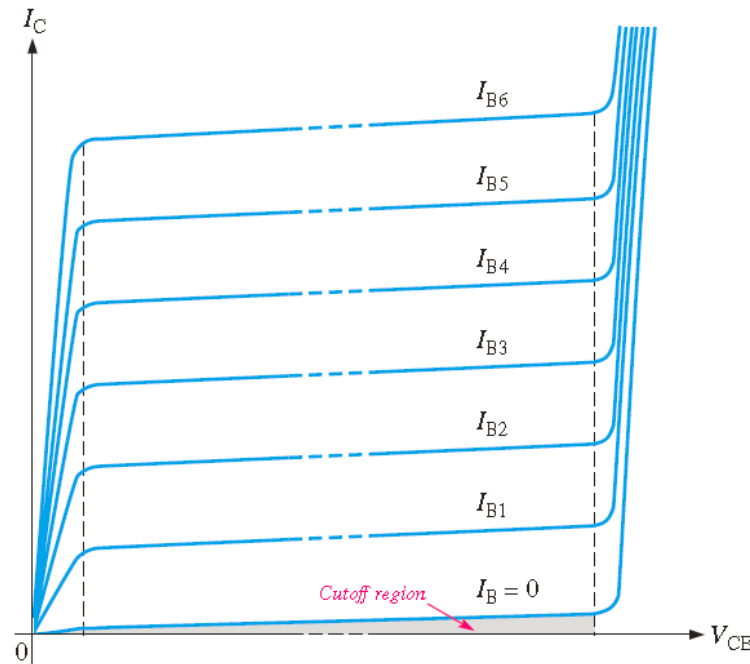
# Collector Characteristic Curves

- Using a circuit like that shown in Figure 4–10(a), a set of collector characteristic curves can be generated that show how the collector current,  $I_C$ , varies with the collector-to-emitter voltage,  $V_{CE}$ , for specified values of base current.



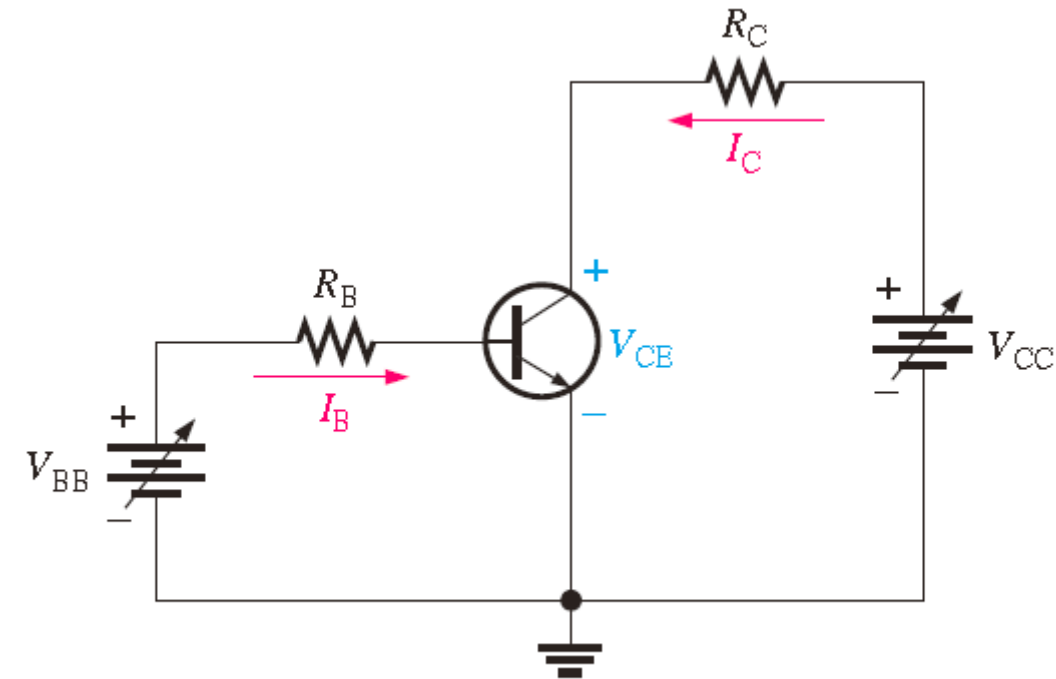(c) Family of  $I_C$  versus  $V_{CE}$  curves for several values of  $I_B$   
( $I_{B1} < I_{B2} < I_{B3}$ , etc.)



(a) Circuit


**FIGURE 4-10**

Collector characteristic curves.



# Collector Characteristic Curves

- $V_{CE}$  is near 0 V. When both junctions are forward-biased, the transistor is in the **saturation** region of its operation. Saturation is the state of a BJT in which the collector current has reached a maximum and is independent of the base current.
- As  $V_{CC}$  is increased,  $V_{CE}$  increases as the collector current increases. This is indicated by the portion of the characteristic curve between points A and B in Figure 4–10(b).
- $I_C$  increases as  $V_{CC}$  is increased because  $V_{CE}$  remains less than 0.7 V due to the forward-biased base-collector junction.

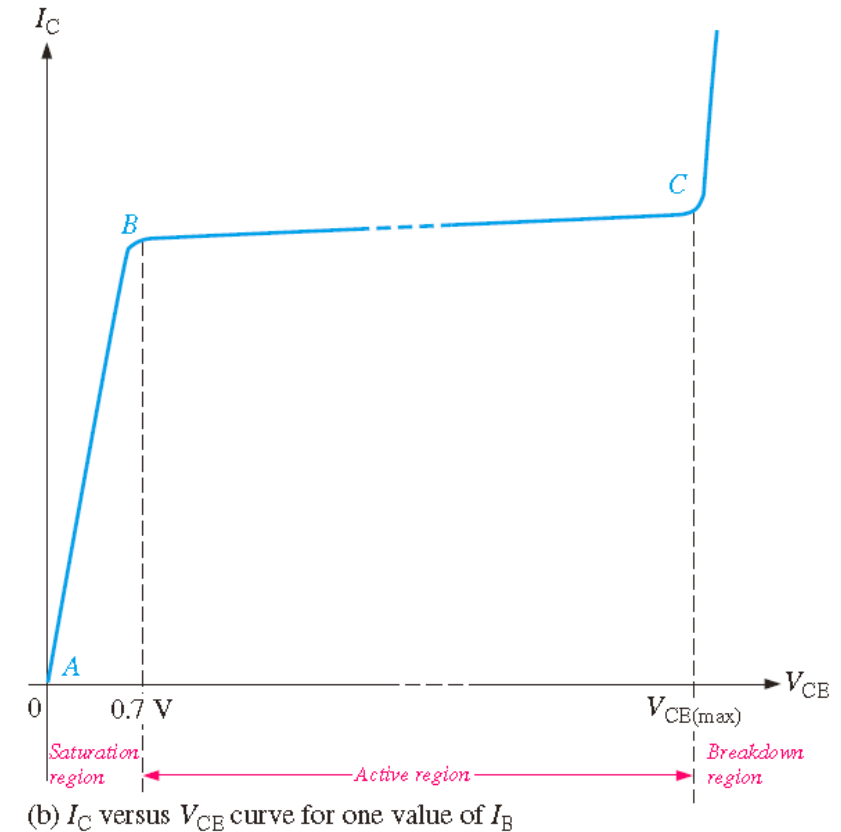


**FIGURE 4-10**

Collector characteristic curves.

# Collector Characteristic Curves

- Ideally, when  $V_{CE}$  exceeds 0.7 V, the base-collector junction becomes reverse-biased and the transistor goes into the active, or linear, region of its operation.
- Once the base collector junction is reverse-biased,  $I_C$  levels off and remains essentially constant for a given value of  $I_B$  as  $V_{CE}$  continues to increase.
- This is shown by the portion of the characteristic curve between points B and C in Figure 4–10(b). For this portion of the characteristic curve, the value of  $I_C$  is determined only by the relationship expressed as
  - $I_C = \beta_{DC} I_B$ .

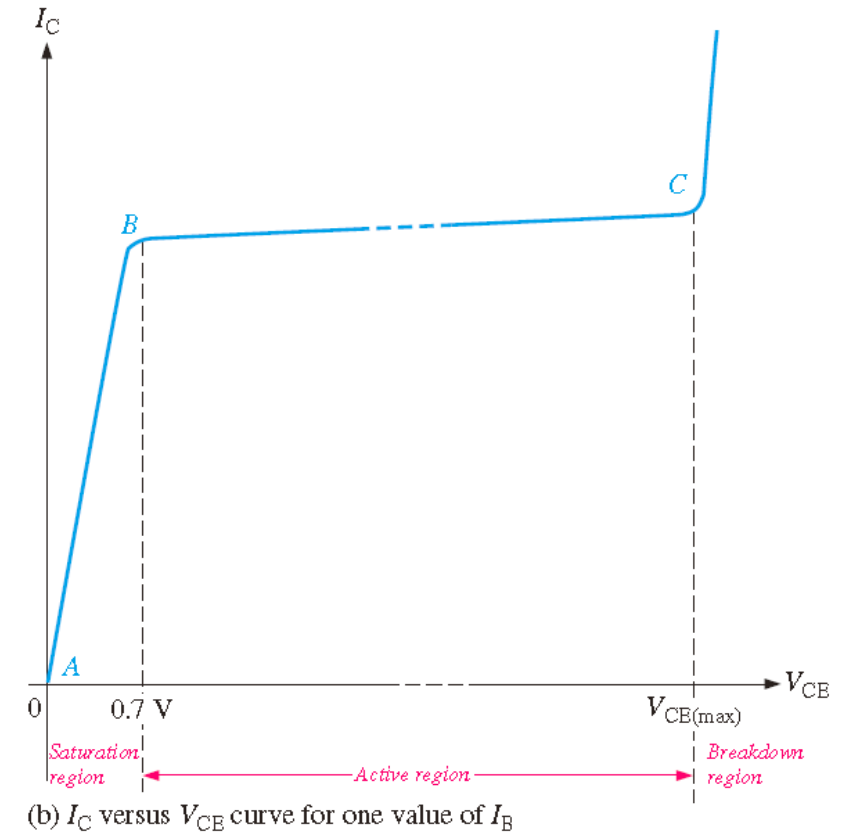


**FIGURE 4-10**

Collector characteristic curves.

# Collector Characteristic Curves

- When  $V_{CE}$  reaches a sufficiently high voltage, the reverse-biased base-collector junction goes into breakdown; and the collector current increases rapidly as indicated by the part of the curve to the right of point C in Figure 4–10(b). A transistor should never be operated in this **breakdown region**.
- When  $I_B = 0$ , the transistor is in the **cutoff region** although there is a very small collector leakage current as indicated. Cutoff is the nonconducting state of a transistor.

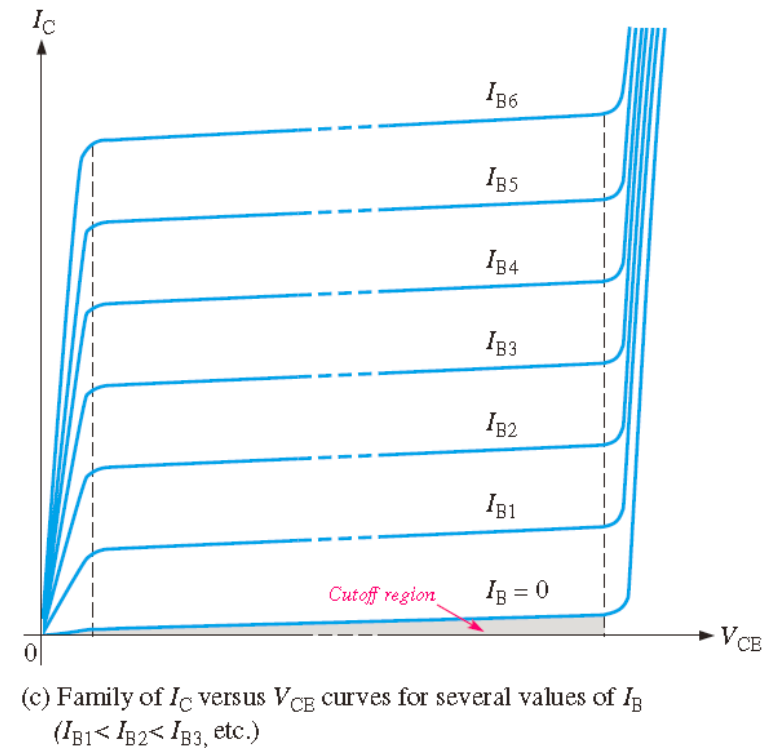


**FIGURE 4-10**

Collector characteristic curves.

# Cutoff

- As previously mentioned, when  $I_B = 0$ , the transistor is in the cutoff region of its operation. This is shown in Figure 4–13 with the base lead open, resulting in a base current of zero.
- Under this condition, there is a very small amount of collector leakage current,  $I_{CEO}$ , due mainly to thermally produced carriers. Because  $I_{CEO}$  is extremely small, it will usually be neglected in circuit analysis so that  $V_{CE} = V_{CC}$ . In cutoff, neither the base-emitter nor the base-collector junctions are forward-biased.

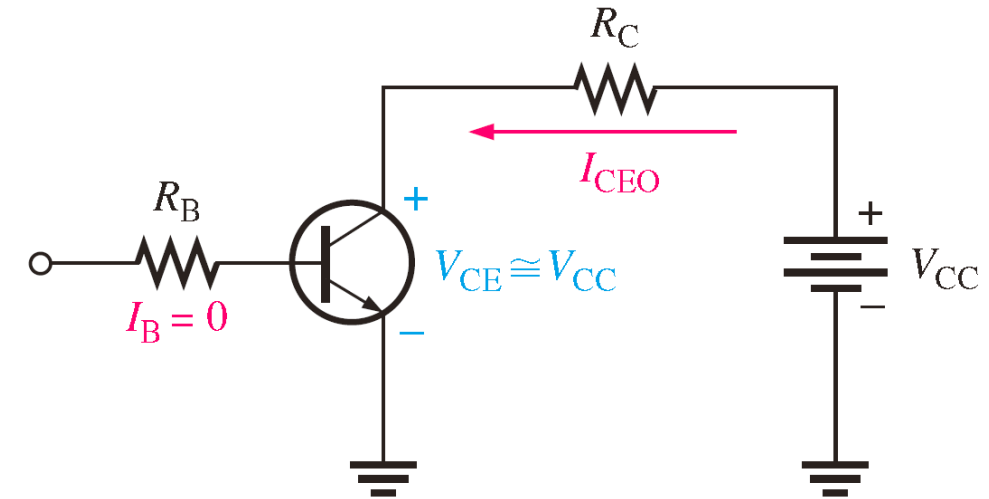


**FIGURE 4-11**

Cutoff: Collector leakage current ( $I_{CEO}$ ) is extremely small and is usually neglected. Base-emitter and basecollector junctions are reverse-biased.

# Cutoff

- When the base-emitter junction becomes forward-biased and the base current is increased, the collector current also increases ( $I_C = \beta_{DC} I_B$ ) and  $V_{CE}$  decreases as a result of more drop across the collector resistor ( $V_{CE} = V_{CC} - I_C R_C$ ). This is illustrated in Figure 4–12.
- When  $V_{CE}$  reaches its saturation value,  $V_{CE(sat)}$ , the base-collector junction becomes forward-biased and  $I_C$  can increase no further even with a continued increase in  $I_B$ .
- At the point of saturation, the relation  $I_C = \beta_{DC} I_B$  is no longer valid.  $V_{CE(sat)}$  for a transistor occurs somewhere below the knee of the collector curves, and it is usually only a few tenths of a volt.

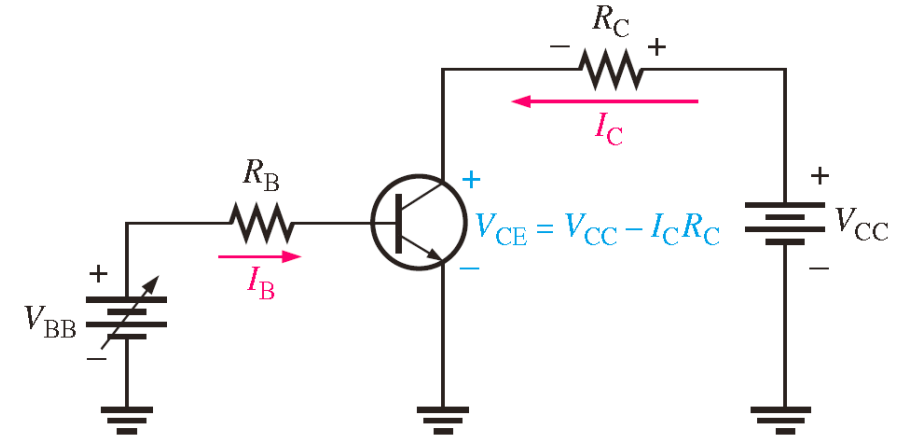

**FIGURE 4-12**

Saturation: As  $I_B$  increases due to increasing  $V_{BB}$ ,  $I_C$  also increases and  $V_{CE}$  decreases due to the increased voltage drop across  $R_C$ . When the transistor reaches saturation,  $I_C$  can increase no further regardless of further increase in  $I_B$ . Base-emitter and base-collector junctions are forward-biased.